


Basic Electronics

The Hydraulic Analogy

Curt Schurgers

UC San Diego
Electrical and Computer Engineering

Electric Circuits

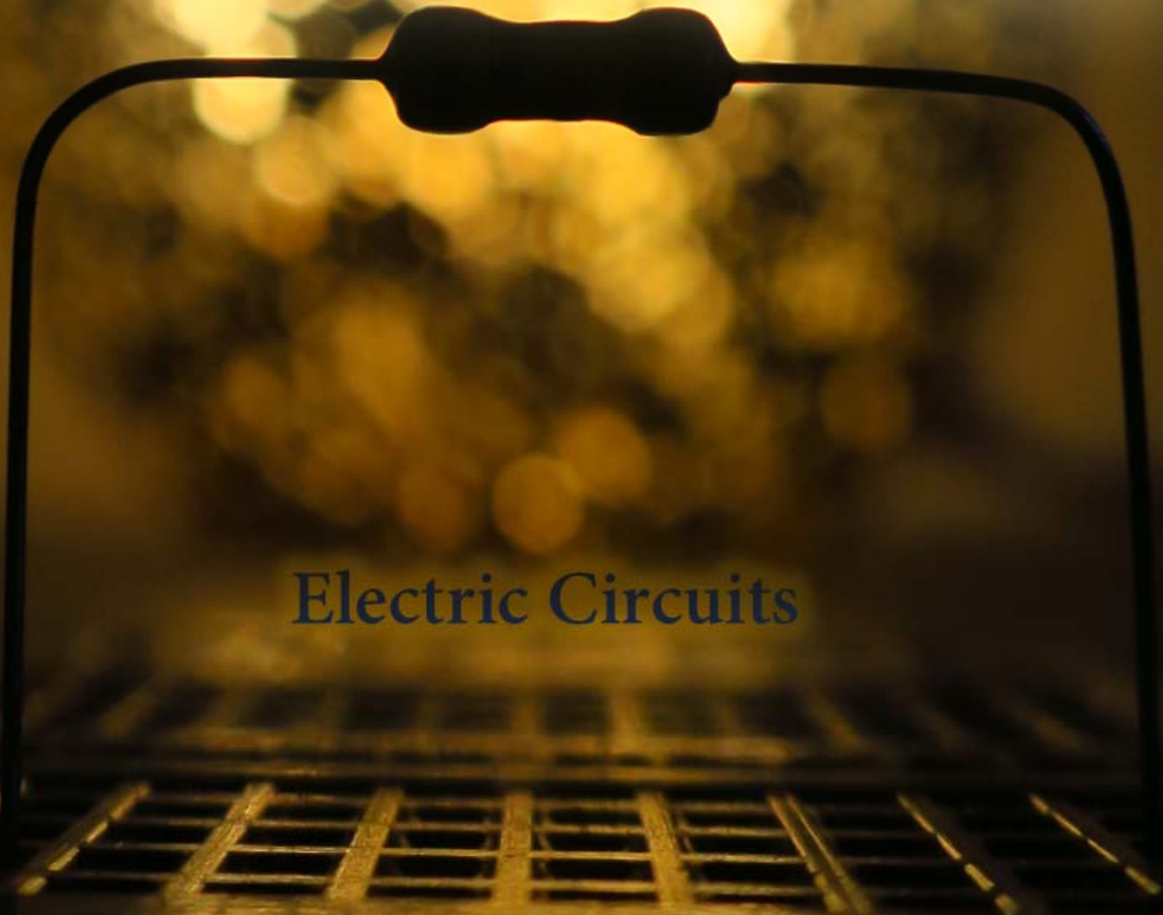

In the hydraulic analogy, electrical circuits are considered analogous to:

[A] buckets of water

[B] water flowing through pipes

[C] water molecules subjected to heat, stirring and turbulence

[D] hydroelectric ocean waves

[E] I don't know

Hydraulic analogy




	Physical quantity	symbol	units
'the flow of particles'	current	I i	ampere (A)
'what pushes'	pressure/voltage	V v	volts (V)
Relationship between the push and the flow	resistance	R	ohm (Ω)

$$V = I \cdot R \quad \text{Ohm's Law}$$

$$\sum_{in} I = \sum_{out} I \quad \text{Kirchhoff's Current Law (KCL)}$$

$$\sum_{up} \Delta V = \sum_{down} \Delta V \quad \text{Kirchhoff's Voltage Law (KVL)}$$

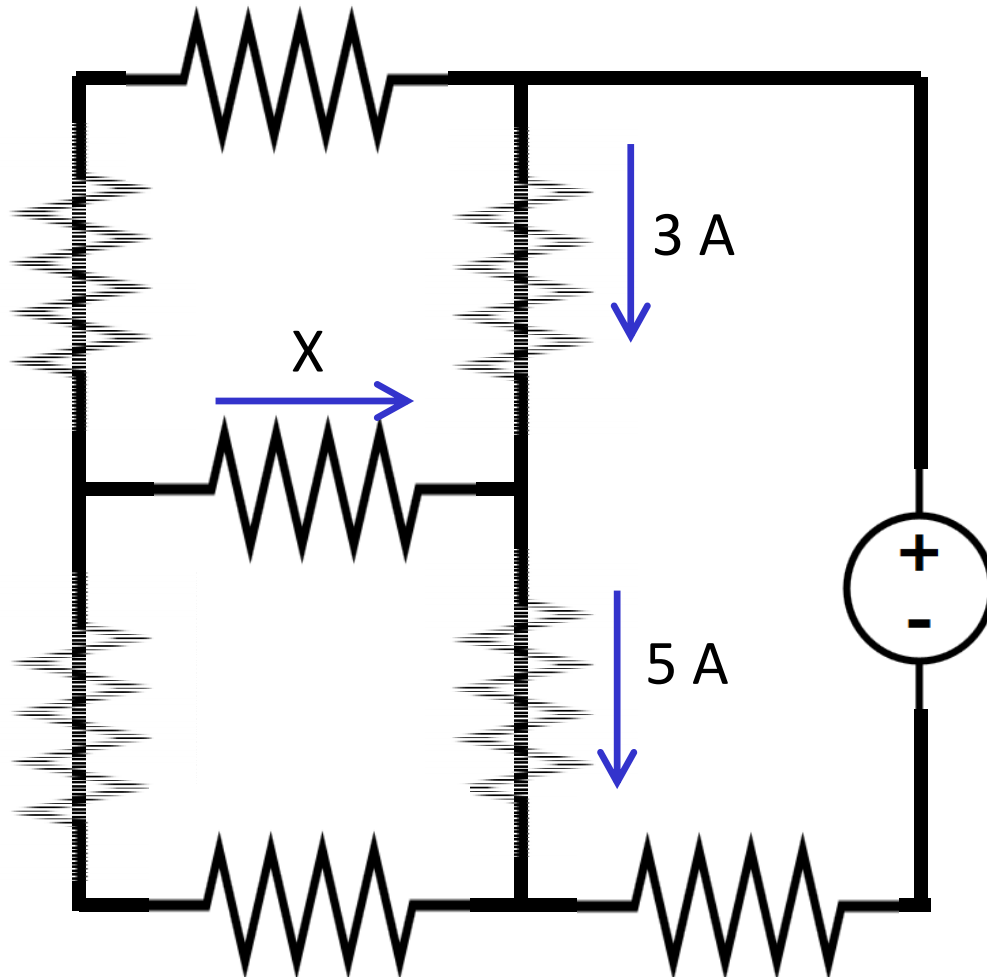If the currents in the various pipes are measured as indicated on the arrows, what is the value of the unknown current X ?



[A] -2 A


[B] 0 A

[C] 1 A

[D] 2 A

[E] I don't know

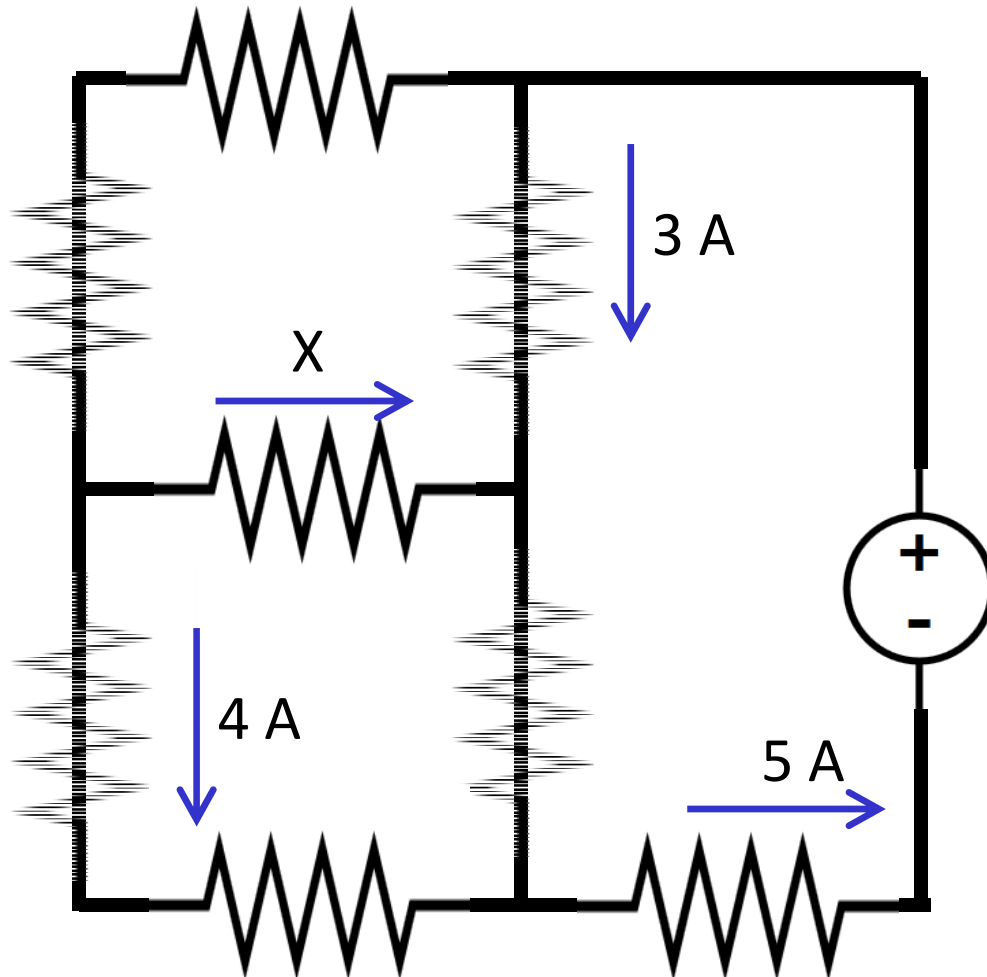If the currents in the various pipes are measured as indicated on the arrows, what is the value of the unknown current X ?



[A] -2 A

[B] 0 A

[C] 1 A

[D] 2 A


[E] I don't know

$$V_a - V_b = 1 \text{ V}$$

$$V_d - V_e = 2 \text{ V}$$

$$V_S = 5 \text{ V}$$

What is the voltage ($V_c - V_d$)?

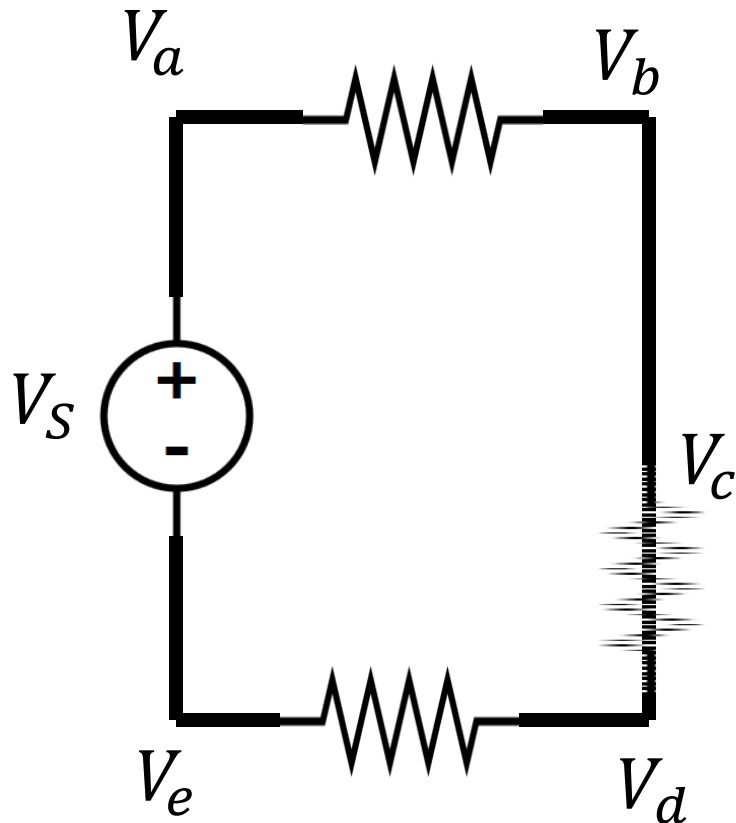

[A] -2 V

[B] 0 V


[C] 2 V

[D] Not enough info
to calculate

[E] I don't know

If the resistance R of the pipe is 2Ω , the current X is:

$$V_S = 8 V$$

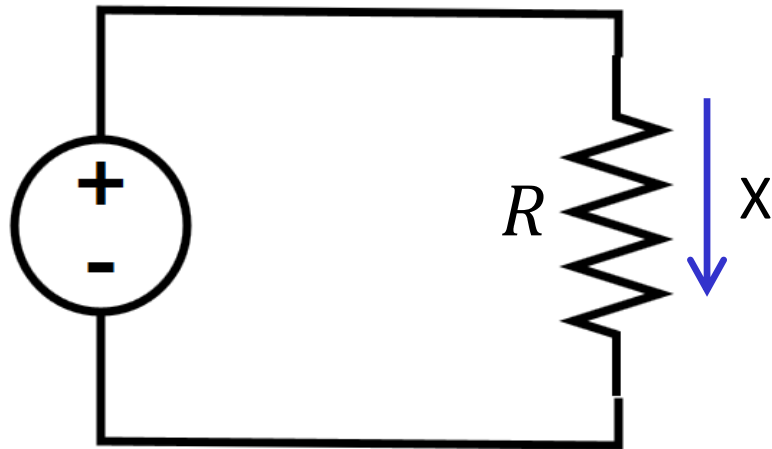


$$V = I \cdot R$$

- [A] 0 A
- [B] 2 A
- [C] 4 A
- [D] 16 A
- [E] I don't know

$$V_a - V_b = 4 \text{ V}$$

$$V_S = 10 \text{ V}$$

What is the voltage ($V_c - V_d$)?

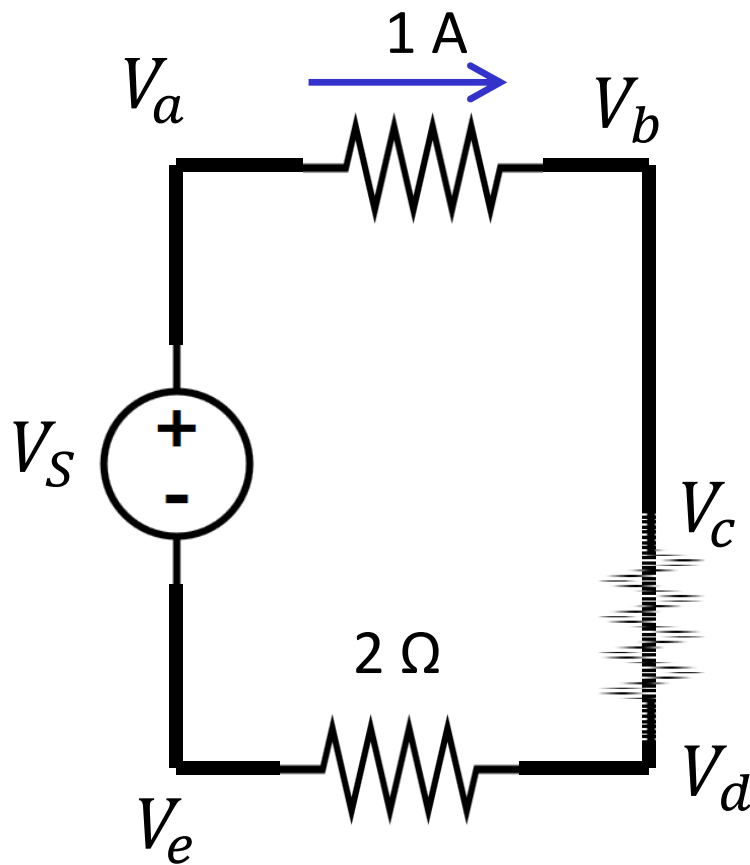

[A] 2 V

[B] 4 V


[C] 6 V

[D] Something else

[E] I don't know

$$V_S = 10 \text{ V}$$

What is the value of node voltage V_C ?

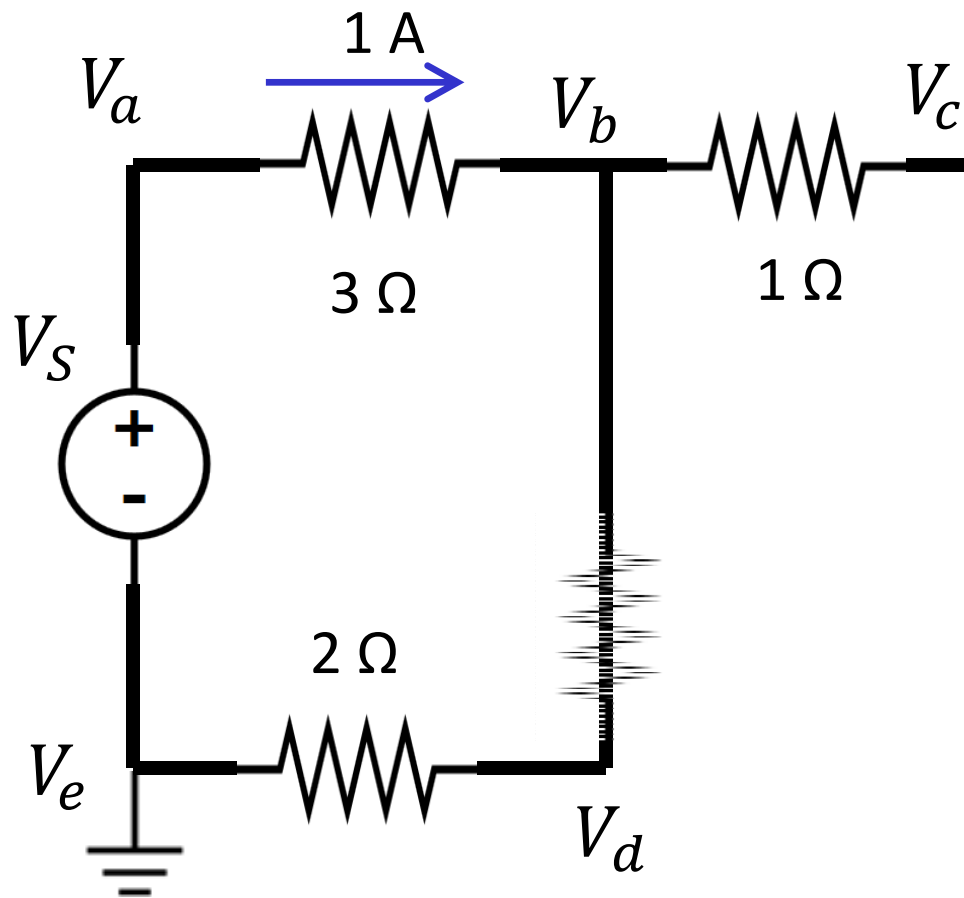

[A] 0 V

[B] 4 V


[C] 6 V

[D] 7 V

[E] I don't know

If the resistance R_1 of the first pipe is 2Ω and the resistance R_2 of the second pipe is 4Ω , the following is true:

$$V_S = 8 V$$

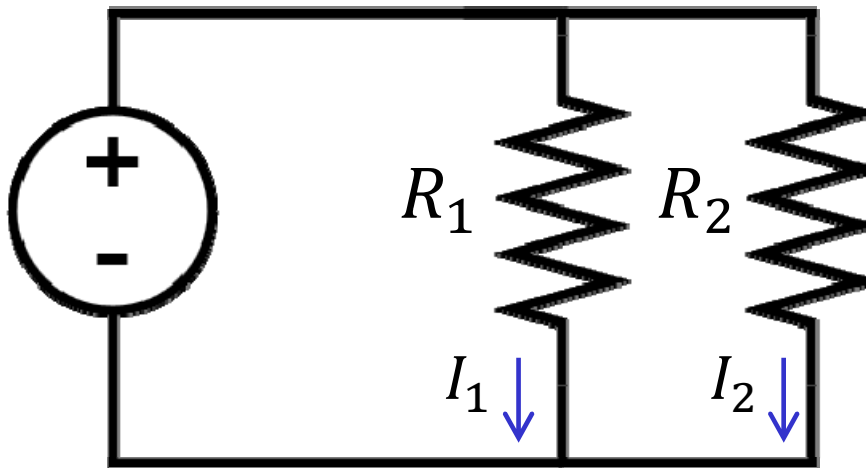


$$V = I \cdot R$$

- [A] $I_1 = I_2 = 0$
- [B] $I_1 = I_2 > 0$
- [C] $I_1 > I_2$
- [D] $I_1 < I_2$
- [E] I don't know

If the resistance R_1 of the first pipe is $2\ \Omega$ and the resistance R_2 of the second pipe is $4\ \Omega$, the total current I coming out of the source (pump) is:

$$V_S = 8\ V$$

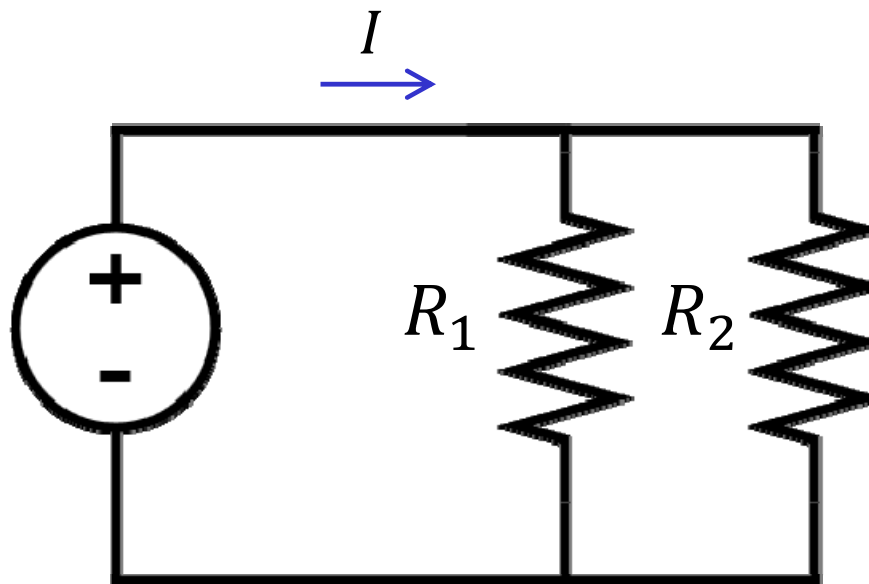

$$V = I \cdot R$$


[A] 3 A

[B] 6 A

[C] 8 A

[D] 48 A

[E] I don't know

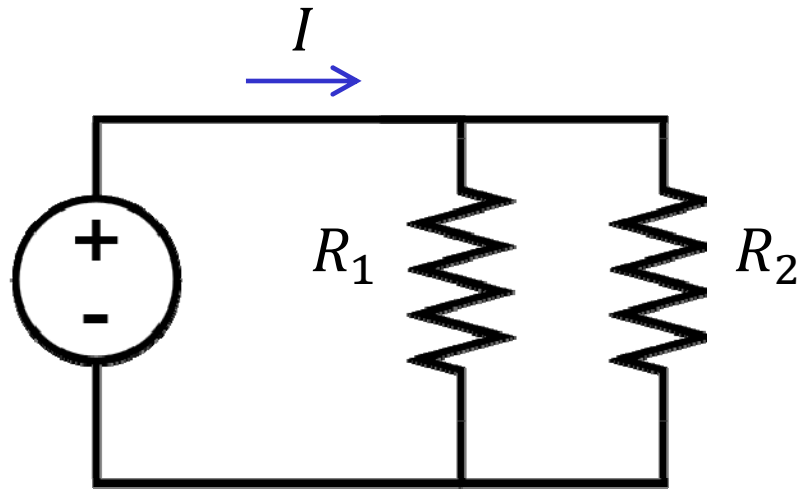


$$V_S = 8 \text{ V}$$

$$R_1 = 2 \Omega$$

$$I = 6 \text{ A}$$

$$R_2 = 4 \Omega$$

Parallel connection

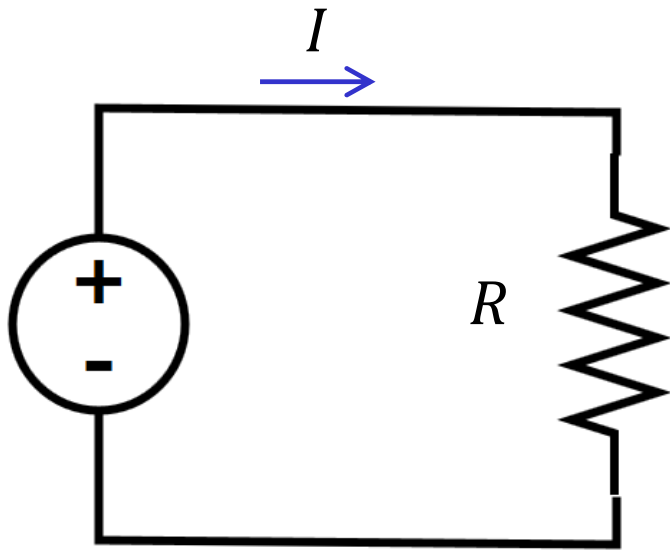


$$V = I \cdot R$$

If the resistance R_1 of the first pipe is 1Ω and the resistance R_2 of the second pipe is 4Ω , the current I coming out of the source (pump) is:


Series connection

$$V_S = 10 \text{ V}$$

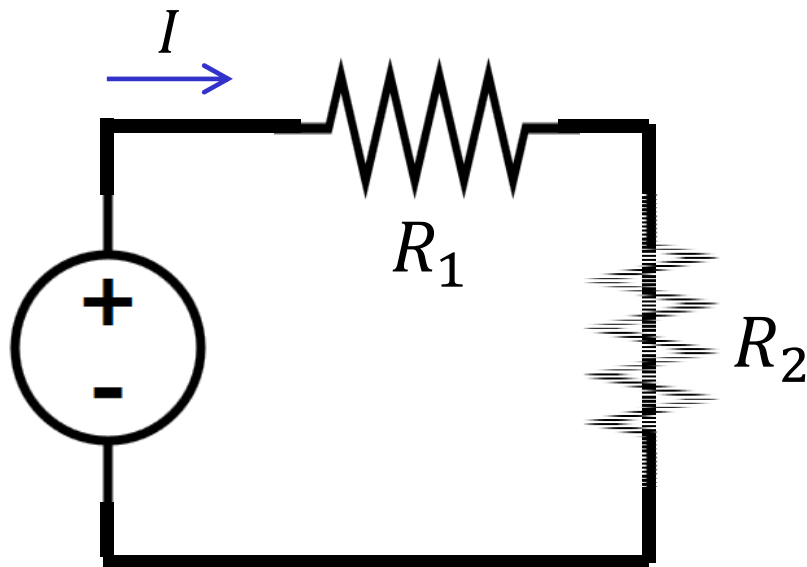

$$V = I \cdot R$$

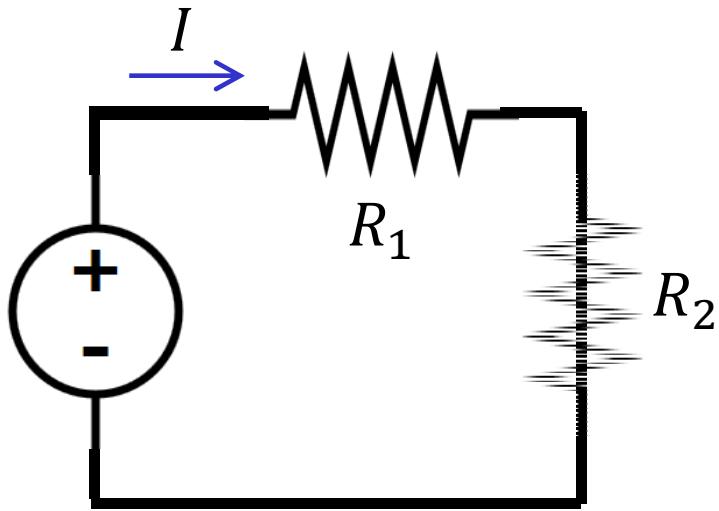- [A] 2 A
- [B] 12.5 A
- [C] 14 A
- [D] 50 A
- [E] I don't know




$$V_S = 10 \text{ V}$$


$$R_1 = 1 \Omega \quad I = 2 \text{ A}$$

$$R_2 = 4 \Omega$$

Series connection

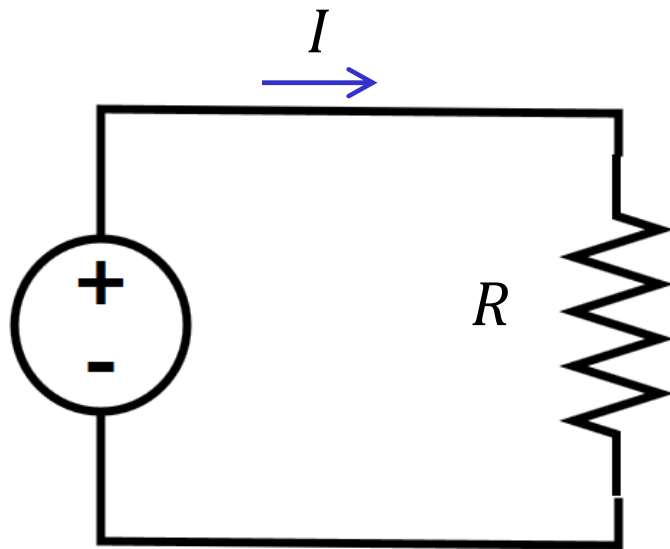


$$V = I \cdot R$$

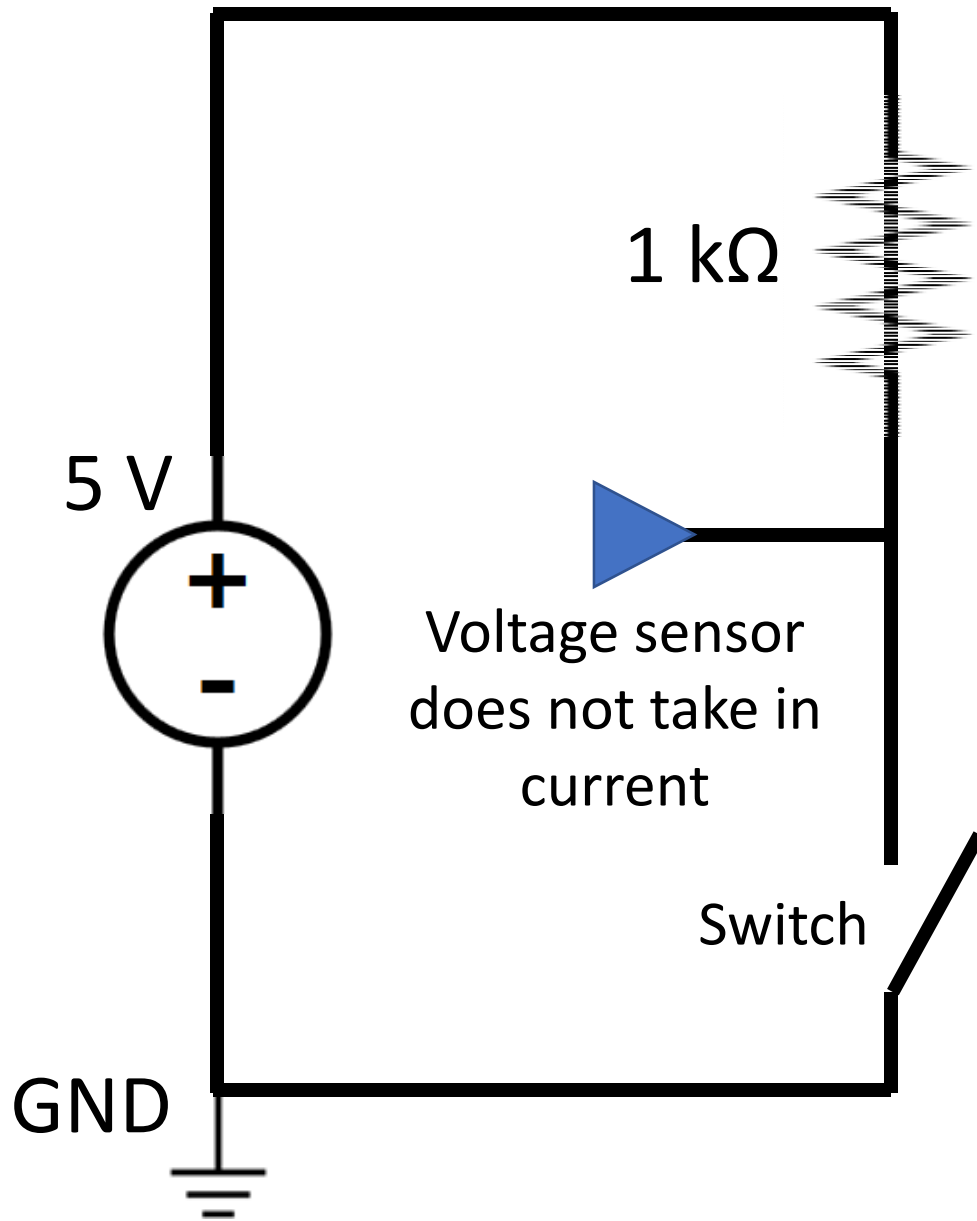

When the switch is open, the voltage measured by the voltage sensor is:

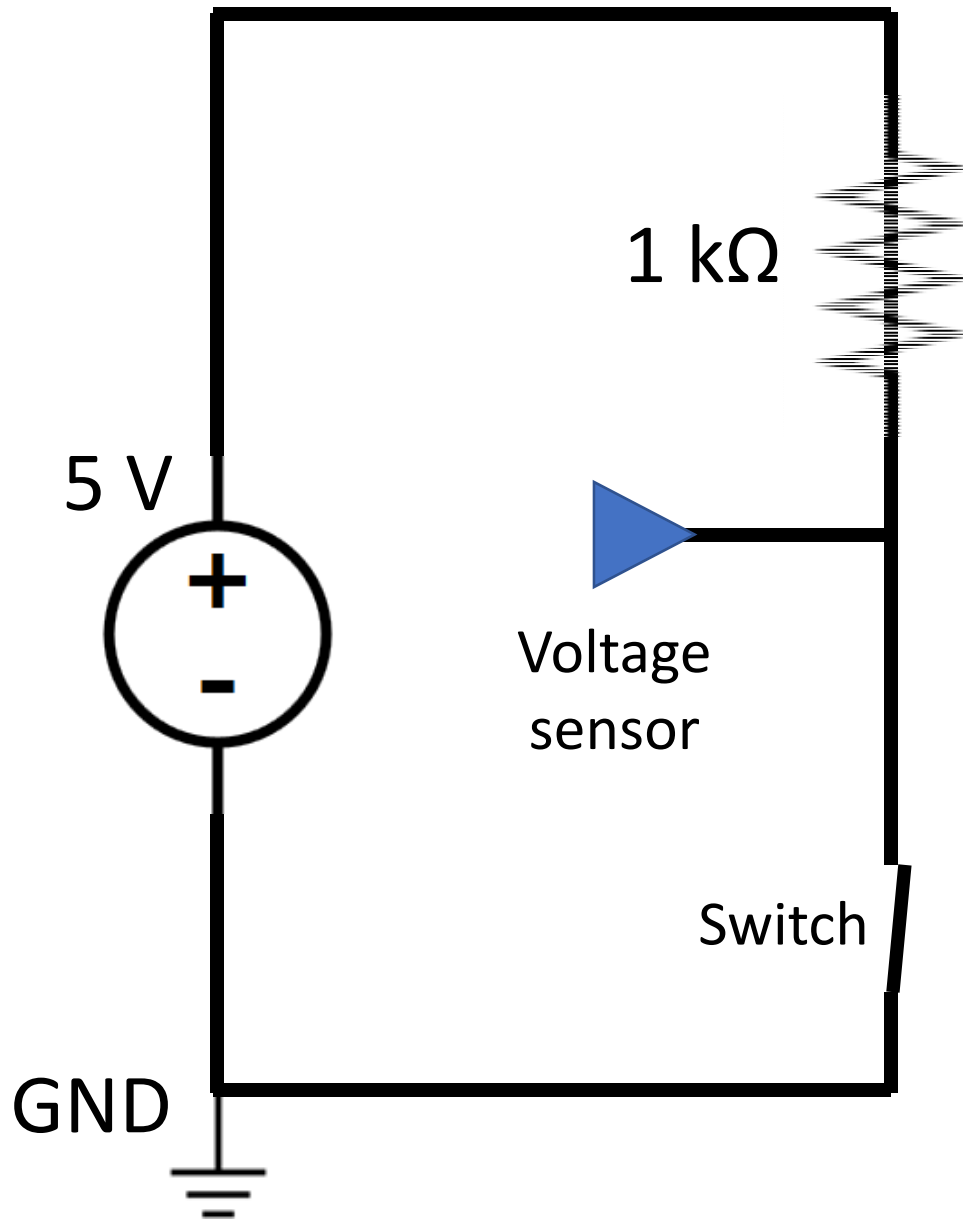- [A] 0 V
- [B] 1 mV
- [C] 1 V
- [D] 4 V
- [E] 5 V



When the switch is closed, the voltage measured by the voltage sensor is:

- [A] 0 V
- [B] 1 mV
- [C] 1 V
- [D] 4 V
- [E] 5 V

What did we learn?

- Pipes correspond to resistors, with certain resistance R
- Wires correspond to ideal pipes, with R very small

- Current only flows in a closed loop
- Voltage over an element is what matters
- Current splits in branches
- Voltage gains and drops in a loop have to add to zero
- Ohm's law: $V = IR$